


Comparator:-

Single supply

Dual supply


Single supply LM 324 for on/off

32V or 30V used

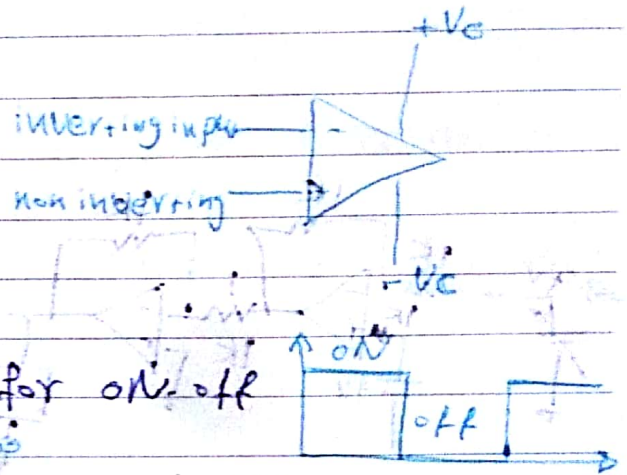

$$\text{if } V_2 > V_1 \Rightarrow V_{out} = 5V$$


$$V_1 > V_2 \Rightarrow V_{out} = -0V$$

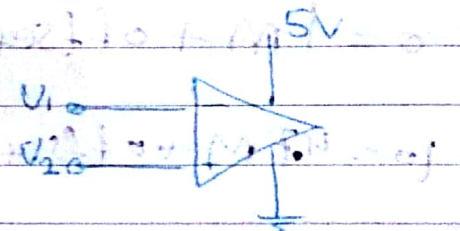

at normal operation amp :-

$$\text{if } V_1 = V_2 \Rightarrow V_o = 0.5 \times [V_{cc} - V_{ref}] = 0.5 \times [5V - 0V] = 2.5V$$
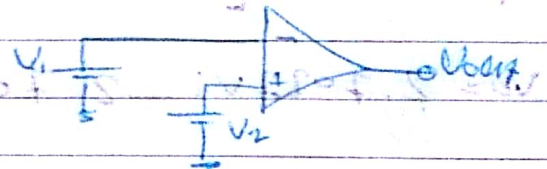
$$V_1 > V_2 \Rightarrow V_{out} = -2.0V$$




$$V_2 > V_1 \Rightarrow V_{out} = 2.0V$$

Ex:- Design a ct that activate a Fan when the temp is exceeded $45^\circ C$ using RTD which sensity is $8.5 \mu V/^\circ C$, $R_1 = 1k\Omega$, $V_{cc} = 5V$

$$V = 5 \times \frac{R_2}{R_1 + R_2} \Rightarrow R_2 =$$

$$\text{if } V_{RTD} > 0.225 \quad V_o = 5V$$

$$< \quad V_o = 0V$$

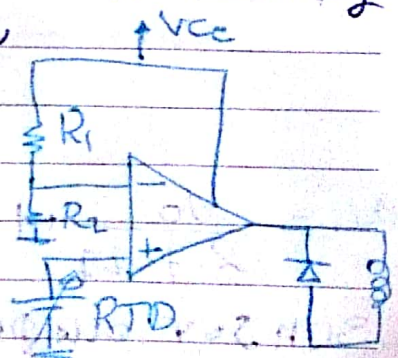

EE 463


Comparator:-

Singl supply

Dual supply

Single supply


أنواع التنبؤ

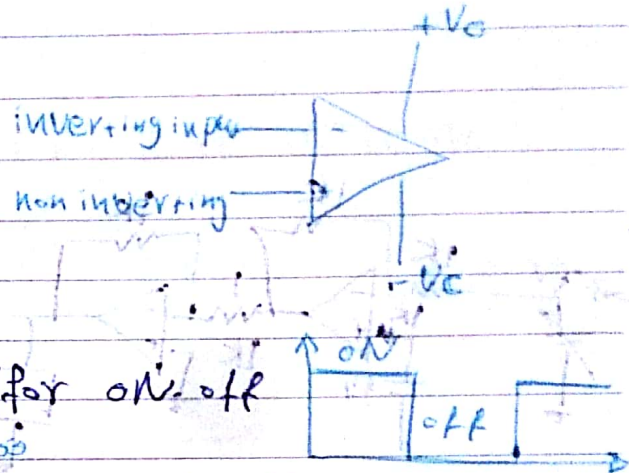

Lin 324 for on/off
32V أو 30V أو 50V

if $V_2 > V_1 \Rightarrow V_{out} = 5V$


$V_1 > V_2 \Rightarrow V_{out} = -0V$

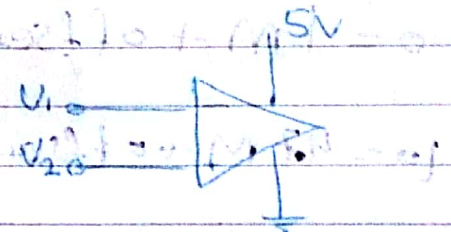

at normal operation amp:-

if $V_1 = V_2 \Rightarrow V_0 = 0$

$V_1 > V_2 \Rightarrow V_{out} = 20V$

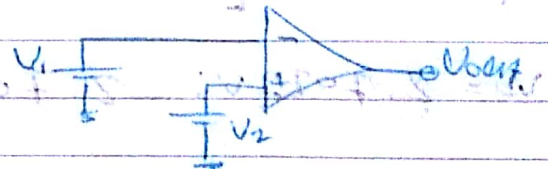


$V_2 > V_1 \Rightarrow V_{out} = 20V$

Ex:- Design a ct that activate a Fan when the temp is axcessed $45^\circ C$ using RTD which sensity is $8.5 \mu V/^\circ C$, $R_1 = 1K\Omega$, $V_{cc} = 5V$

$$V = 5 \times \frac{R_2}{R_1 + R_2} \Rightarrow R_2 = \frac{V(R_1 + R_2)}{5 - V}$$

if $V_{RTD} > 0.325 \Rightarrow V_0 = 5V$

$V_0 = 0V$

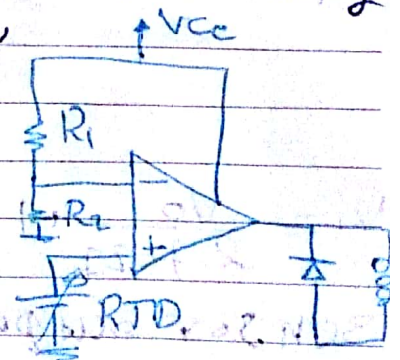

EE463

Ex:- Design a ckt that activate a Hecter when the temp is less than 20°C using RTD which sensitivity $8.5\text{mV}/^{\circ}\text{C}$


Sols:-

at 20°C

$$V = 20 \times 8.5 = 0.17$$

$$R_1 = 1\text{K}\Omega$$

$$R_2 = 55\text{K}\Omega$$

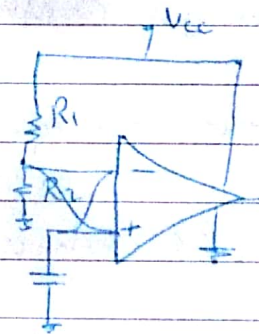

Regulator:-


7805 $+5\text{V}$

7812 $(+12\text{V})$

7905 (-5V)

7912 (-12V)

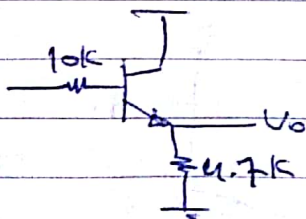Q1: Zener 5V and 20mA is used
with a Heat Sink



Buffer.

inverter.

EE 463

Full up and full down \rightarrow (Floor) لرفع حالة الطفو

Ex:- design control circuit to turn ON RED LED


When the temperature is more than 36°C ? & turn on

Blue LED when temperature is less than 19°C

and turn on Green LED when the temp is

between them [Use LM35] $10 \text{ mV}/^\circ\text{C}$

at $36^{\circ}\text{C} \rightarrow \text{sensor output} = 360\text{mV}$
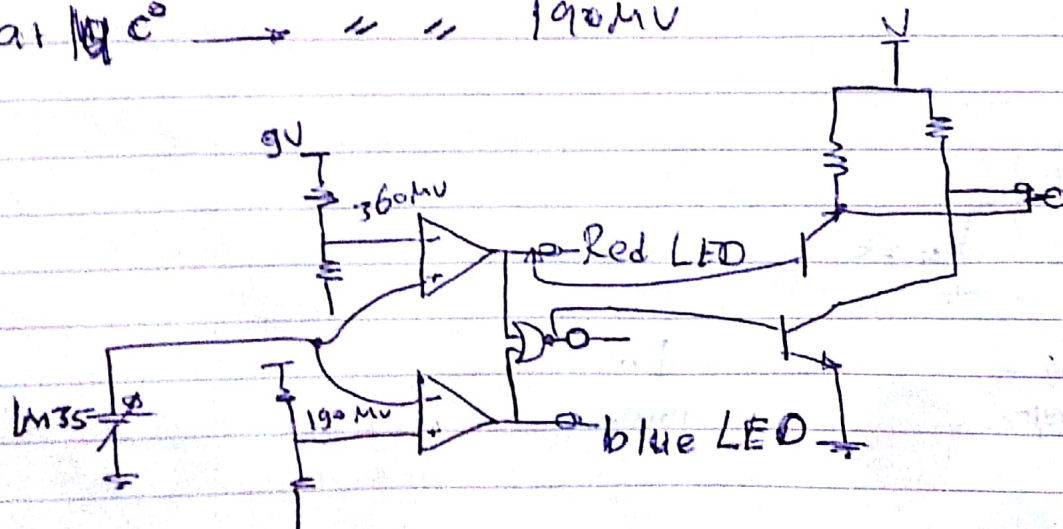
$$a_1 \approx 10^6 \rightarrow \approx \approx 190 \mu V$$


* Filters:-

passive filters.

Ex:- low pass filter (LPF)


High pass filter (HPF)

Band pass Filter (BPF)

Band stop Filter (BSF)

low pass RC Filter:-

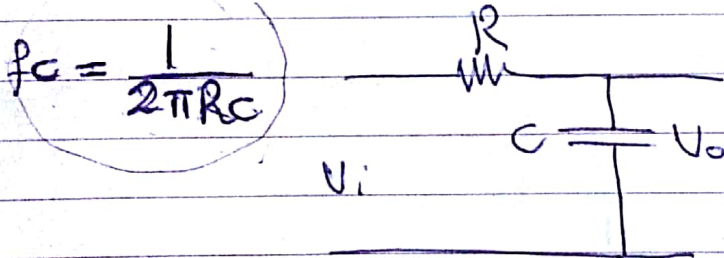because it blocks high freq and passes low freq
 Critical freq or cutoff Freq:- is that freq for which
 that ratio of the output to the input voltage is
 approximately 0.707



Ex:- A measurement signal has a freq $< 1\text{ kHz}$ but there is unwanted noise at about 1 MHz . Design low pass filter that attenuate the noise 1% What is the effect on measurement signal at the maximum of 1 kHz

$$\frac{V_o}{V_i} = \frac{1}{\sqrt{1 + \left(\frac{1M}{f_c}\right)^2}}$$

الشارة
تشويش

$$\frac{1}{100} = \frac{1}{\sqrt{1 + \left(\frac{1M}{f_c}\right)^2}}$$

$$1 + \left(\frac{1MHz}{f_c}\right)^2 = 10000$$

$$\left(\frac{1MHz}{f_c}\right)^2 = 9999$$

$$\frac{1MHz}{f_c} = \sqrt{9999} \Rightarrow f_c = 10.0005 \text{ KHz}$$

$$f_c = \frac{1}{2\pi RC}$$

$$\text{let } C = 0.47 \mu F, f_c = \frac{1}{2\pi RC}$$


$$R = 33.9 \Omega$$

$$\text{let } C = 0.01 \mu F \Rightarrow R = 1591 \Omega$$

المقاومة الموجودة في السوق 1500

$$f_c = 10.61 \text{ KHz}$$

EE 463

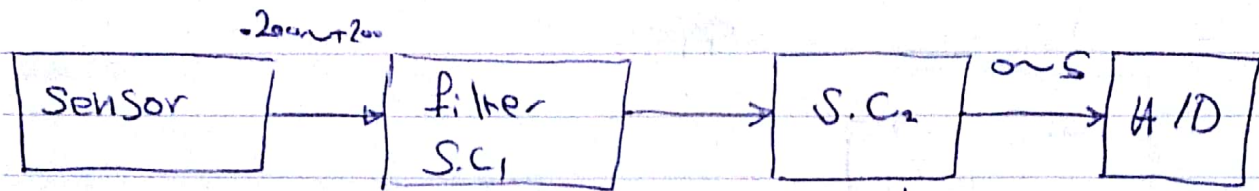

$$0 = -190 \text{ mV} + 0 \text{ fset}$$


$$\underline{-190.8 \sim 190.8}$$

$$V_0 = V_i / 13.15 + 2.5$$

$$5 = 190 \text{ mV} \cdot M + 0 \text{ fset}$$


$$5 = 0.380 \text{ m} \Rightarrow M = 13.15 \text{ m}$$

$$0 \text{ fset} = 2.5$$

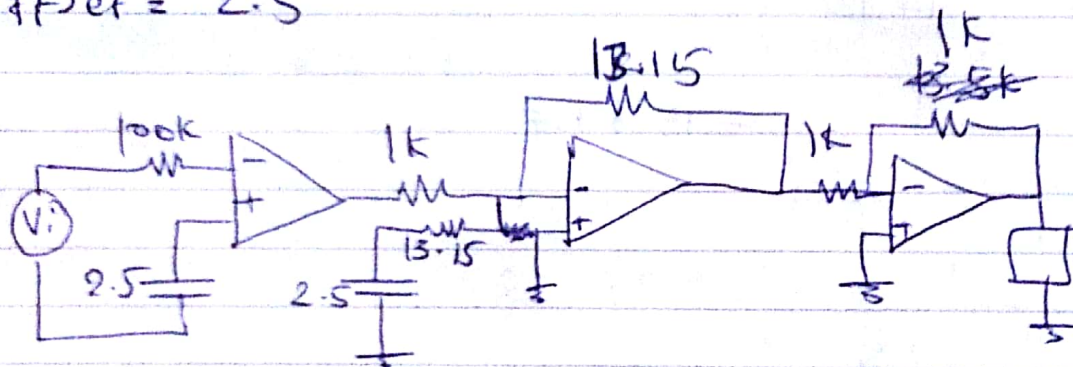

Ex:- Design signal conditioning circuits for the sensor which range -100mV to $+250\text{mV}$ & frequency 5Hz and the noise signal $\rightarrow 20\text{mV}$, frequency 60Hz and attenuation $\rightarrow 30\%$ for ADC ($0 \rightarrow 10$) and we will transmit the data up to 0.3KM

Ans:-

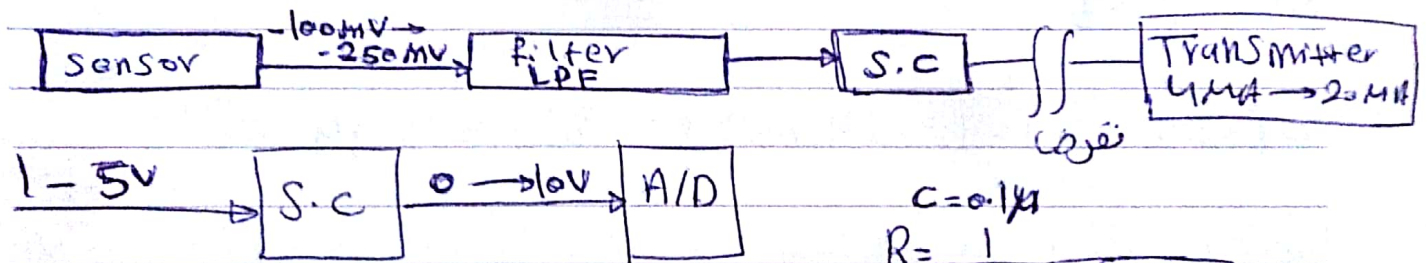

$$C = 0.1\mu\text{F}$$

$$R = \frac{1}{2\pi \times 0.1 \times 10^{-6} \times 18.869}$$

$$= 84.347\text{K}\Omega$$

$$\Rightarrow \frac{30}{100} = \frac{1}{\sqrt{1 + \left(\frac{f_s}{f_c}\right)^2}} \Rightarrow f_c = 18.869$$

$$\frac{V_o}{V_i} = \frac{1}{\sqrt{1 + \left(\frac{f_s}{f_c}\right)^2}} = \frac{V_o}{V_i} = \frac{1}{\sqrt{1 + \left(\frac{5}{18.869}\right)^2}} = 96.66$$

The new ~~sen~~ sensor range after filtering

$$(-96.66\text{mV} \sim +24.659\text{mV})$$

S.C to (1 \rightarrow 5V)

$$\frac{V_o}{V_i} = \frac{1}{\sqrt{1 + \left[\frac{1 \text{ kHz}}{10.61} \right]^2}} = 0.9956$$

$$= \% 99.56 \rightarrow \text{Circuit is working}$$

Ex:- Design S.C for ADC ($0 \rightarrow 5\text{V}$) for sensor range ($-200 \sim +200\text{mV}$) $f_s = 5\text{Hz}$ Noise signal 20mV , $f_N = 50\text{Hz}$

$$\frac{5}{100} = \frac{1}{\sqrt{1 + \left(\frac{50}{f_c} \right)^2}} = 2.5\text{Hz}$$

$$\frac{30}{100} = \frac{1}{\sqrt{1 + \left(\frac{50}{f_c} \right)^2}} = 15.7\text{Hz}$$

$$\frac{V_o}{V_i} = \frac{1}{\sqrt{1 + \left(\frac{5}{15.7} \right)^2}} = \% 95.28$$

$$f_c = \frac{1}{2\pi RC}, \quad C = 0.1\mu\text{F}, \quad R = 101.3\text{k}\Omega$$

$$f_c = \frac{1}{2\pi \times 0.1 \times 10^{-6} \times 100 \times 10^3} = 15.92$$

$$\frac{V_o}{V_i} = 95.4\%$$

S.C (1 \rightarrow 5V)

$$I = 0.09666 M + \text{offset} \rightarrow \textcircled{1}$$

$$I = 0.241659 M + \text{offset} \rightarrow \textcircled{2}$$

$$M = 0.338319 M$$

$$M = 11.82$$

$$\text{offset} = (5) - (0.241659 \times 11.82) = 2.14$$

~~$$V_o = 11.82 V_i + \text{offset}$$~~

$$V_o = 11.82 V_i + 2.14$$

~~$$V_o = V_i$$~~
$$V_o = 11.82 (V_i + 0.18V)$$

S.C to (0 \rightarrow 10V)

$$0 = M + \text{offset}$$

$$10 = 5M + \text{offset}$$

~~$$10 = 11M$$~~
$$\rightarrow M = 2.5$$

$$\text{offset} = -2.5$$

$$V_o = 2.5 V_i - 2.5 \Rightarrow V_o = 2.5 (V_i - 1)$$

Ex: Design signal conditioning circuit for the sensor which range (0mV \rightarrow 250mV) and frequency 1kHz and the noise signal \rightarrow 200mV (frequency 60Hz) choose the proper filter for ADC V_{ref} (0 \rightarrow 10)

$$\frac{V_o}{V_i} = \frac{F_N/f_c}{\sqrt{1 + \left(\frac{f_N}{f_c}\right)^2}} \quad \text{for H.P.F} \quad \begin{array}{c} C \\ | \\ R \end{array} \quad \text{H.P.F}$$

$$f_c = \frac{1}{2\pi R C}$$

مثلاً

Ans:- Assume $\frac{V_o}{V_i} = \text{for noise } 10\%$


$$\frac{10}{100} = \frac{60/f_c}{\sqrt{1 + \left(\frac{60}{f_c}\right)^2}} = f_c = 596. \text{ Hz} \quad \left(\text{تأثير على الإشارة الأصلية} \right)$$

$$\frac{V_o}{V_i} = \frac{1000}{\sqrt{1 + \left(\frac{1000}{596}\right)^2}} = 85\%$$

if attenuation for signal 30%


$$f_c = 190.78 \text{ Hz}$$
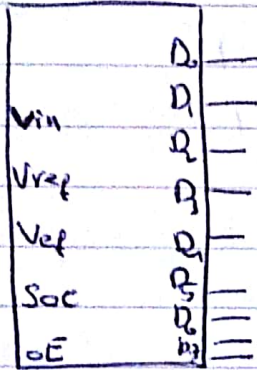
$$\frac{V_o}{V_i} = \frac{1000}{\sqrt{1 + \left(\frac{1000}{190.78}\right)^2}} = 98\% \Rightarrow 98.22$$



نهاية عملية التحويل

End of conversion

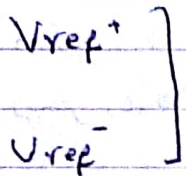

يحدد ونوع قطبية المحول

Unipolar \Rightarrow (0 \rightarrow 5V). (0 \rightarrow 5-)
 bipolar \Rightarrow (5V \pm)

Soc \rightarrow أمر يوافق التحويل
 output enable


$$\Rightarrow \% \Delta V = \frac{1}{2^n} = \frac{1}{2^8} = \frac{1}{256} = 2.5 \times 10^{-3} \Rightarrow \text{عدد العناوين}$$

أقل قيمة يسعها التحويل
 الإشارة

$$\frac{\text{الدقة الدفئلي}}{\Delta V} = \text{الخروج الدققي}$$

EE463

4-12/2017

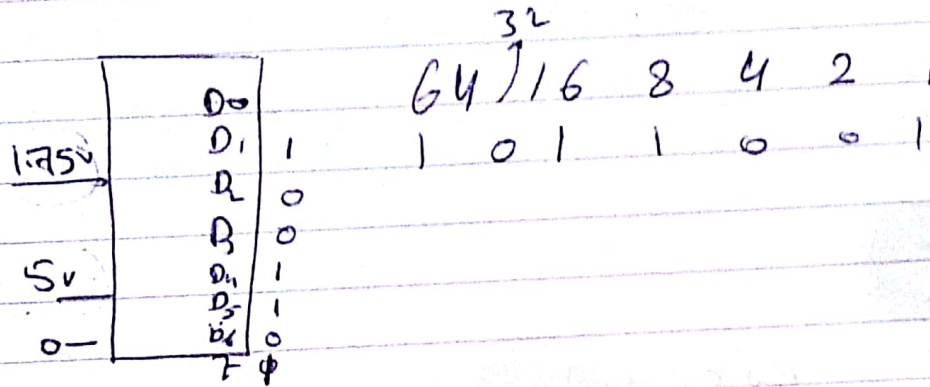

Ex: What is the Volt

$$\Delta V = \frac{5}{2^8} = \frac{5}{256} = 19.531 \text{ mV} \Rightarrow \text{كل ما يحصل 19.531 mV} \\ \text{يغير مقدار واحد}$$

$$\text{slope} = \frac{1.75}{19.531} = 89.609 \approx 90$$

Ex:-

Using pressure sensor which sensitivity 13 mV/bar

design a S.C Circuit to connect it to ADC which

Voltage reference $[0 \rightarrow 5]$ 8 bit Δ (Sensor) $P, \text{ range } (0 \rightarrow 30 \text{ bar})$

What is the ADC output at 10 bar.

Solution: $(0 \rightarrow 13 \times 30)$
 $(0 \rightarrow 390 \text{ mV})$

$$0 = 0 \text{ m} + \text{offset} \Rightarrow \text{offset} = 0$$

$$5 = 0.39 \text{ m} \Rightarrow \text{m} = 12.82$$

$$V_o = V_i 12.82$$

V_i	0	0.195	0.39
V_o	0	2.5	5

$$\Delta V = \frac{5-0}{2^8} = \frac{5}{256} = 19.53125 \text{ mV}$$

B) Sensor output at 10 bar $\Rightarrow 10 \times 13 \text{ mV} = 130 \text{ mV}$


$$D = at$$

EE463

7-12-2017

$$\text{ADC output} = \frac{\text{Analog input}}{\Delta V} = \frac{1.6667}{19.53} = 85.35$$

$$= 85$$

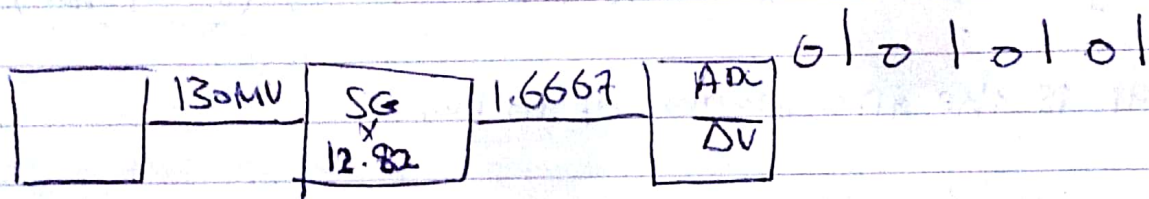

Ex:-

Using pressure sensor which sensitivity 0.24 mA/bar

in the range $0 \rightarrow 10 \text{ bar}$ and its input @ 0 bar 12 mA


Design S.C circuit to connect it to ADC 8 bit which reference $(0 \rightarrow 6 \text{ V})$.

What is the ADC output (5.5 bar).

(range sensor):-

$$(0 \rightarrow 10 \times 0.24 \text{ mA}) = 12 \text{ mA} \rightarrow 12 \text{ mA} + (10 \times 0.24 \text{ mA} / \text{bar})$$

$$\rightarrow (12 \text{ mA} \rightarrow 14.4 \text{ mA})$$

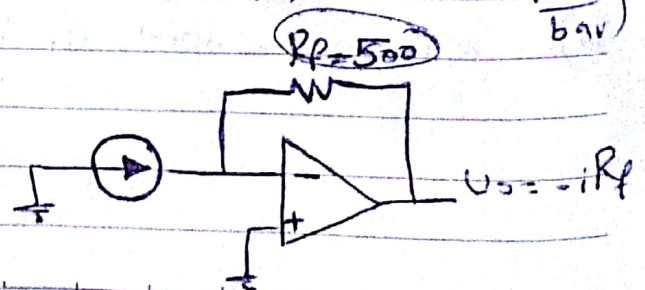

EE 463

7-12-2017

$$12 \text{ mA} \times 500 = 6 \text{ V}$$

$$14.2 \text{ mA} \times 500 = 7.2 \text{ V}$$

$$\text{Rang}(V) = (6 \rightarrow 7.2) \text{ V} \quad [2 \text{ se aqee Chel}]$$


$$0 = 6 \text{ M} + \text{offset}$$

$$6 = 7.2 \text{ M} + \text{offset}$$

$$6 = 1.2 \text{ M} \rightarrow \text{M} = \frac{6}{1.2} = (5) \quad \text{offset} = -30$$

$$V_o = 5V_i - 30$$

$$V_o = 5(V_i - 6)$$

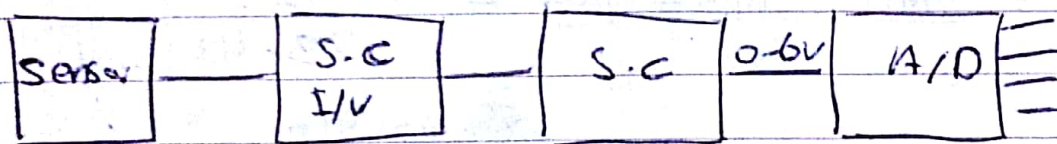

$$\Delta V = \frac{6-0}{28} = 0.214285$$

$$\text{at } 5.5 \text{ bar} \quad 5.5 \times 0.24 \times 12 = 13.32 \text{ MA}$$

$$-(13.32 \text{ MA} \times 0.5 \text{ k}) = -6.66 \text{ V}$$


$$V_o = 5(6.66 - 6) = 3.3 \text{ V}$$

$$\text{digital output} = \frac{3.3}{23.4375} = 140, 1000/100$$

EE463

7-12-2017

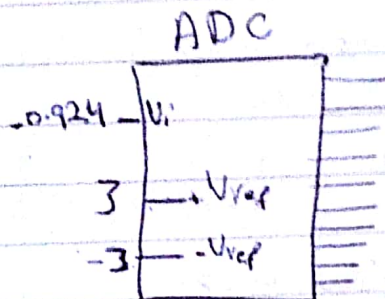Ex.: What is the digital output of the following



$$\Delta V = \frac{V_{ref(+)} - V_{ref(-)}}{2^n} = \frac{6}{256} = 23.4375 \text{ mV}$$

$$\text{Dig output} = \frac{\text{Analog input} + V_{ref}}{\Delta V} = \frac{-0.924 + 3}{23.4375 \text{ mV}}$$

$$88 = 01011000_2$$

$$\Delta V = \frac{8}{2^6} = 0.03125$$

$$\text{Digital output} = 170.24 = 170 = 10101010_2$$

S.

Using an Acceleration which Sensitivity $\pm 20g$ (10mV/g)

Design circuit for ADC which reference $\pm 5V$ (8 bit)

& which is output of ADC at $+3g$ & $-7g$

sensor rang ($-200mV$ - $200mV$)

$$-5 = -200mV + \text{offset}$$

$$5 = 200mV + \text{offset}$$

$$10 = 400mV \Rightarrow m = \frac{10 \times 1000}{400} = 25$$

$$V_o = V_i \times 25$$

Digital output at $3g$

$$\Delta V = \frac{5 - (-5)}{2^8} = \frac{10}{2^8} = \frac{10}{256} = 39.0625mV$$

$$\text{Digital output} = \frac{\Delta V}{V_{ref}(+)} = \frac{0.75 + 5}{39.0625 \times 10^{-3}} = 147.2 = 147 = (10010011)_2$$

33

band pass

$$(39 \times 10mV/g)(25) = 0.75$$


Sensor outputs

$$at -79 = -70mV$$

$$\text{Analog input} = -70 \times 95 = -1.75V$$

$$\text{Digital output} = \frac{-1.75 + 5}{39.0625 \times 163}$$

$$183 = 01010011$$

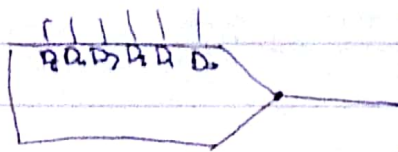

analog output


$$\Delta V = \frac{V_{ref}}{2^n} = \frac{3}{2^8} = 0.0117$$

↓
الخطوة (resolution) ← أقل قيمة يستجيب لها التحويل

الخطوة الرقمية . المخرج التماثلي

$$\text{Analog output} = \text{Digital input} \times V_{ref} \times \Delta V$$

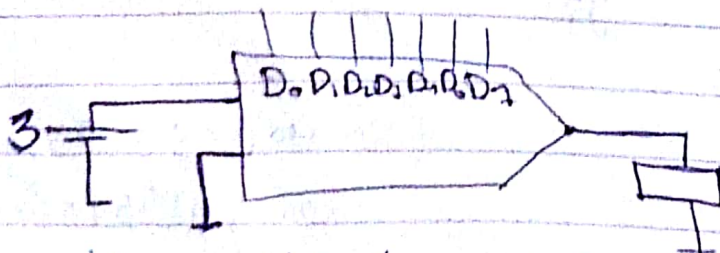Ex:- what is the analog output value of the following ADC



$$10100011, 163 \times 0.01171875 = 1.91V$$

What is the output volt of (10 bit) DAC Unipolar 10V ref
if the input is $A = 0B5H$

$$B = 20FH$$

What is the input needed to get 6.5V (o/p)

$$\Delta V = \frac{10}{2^0} = \frac{10}{1024} = 9.765 \text{ mV}$$


$$\text{Analog output} = \text{Dig input} \times \Delta V = 527 \times 9.765 \times 10^3 = 5.1 \text{ V}$$

0B5H

$$0010110101 \rightarrow 181X$$

* bipolar example:-
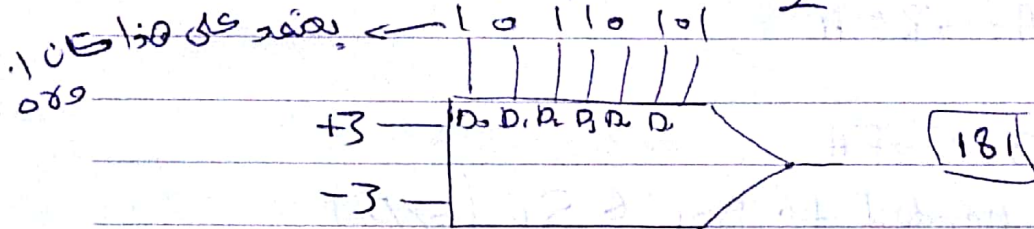
$$V_o = (\text{Digital input} \times DV) - \frac{V_{REF}}{2}$$



$$V_0 = \underline{181} \times 23.4375 \times 10^{-3} - 3 = 1.24 \text{ V}$$

$$\Delta V = \frac{3 - (-3)}{2^8} = \frac{6}{2^8} = 23.4375 \mu V$$

Ex:- Using Temp sensor which sensitivity $0.3 \text{ mA}/^\circ\text{C}$


8) pressure sensor which sensitivity 4.2 mV/bar design

Circuit which operate Fgh at temp is 35°C

and oprray value. if Pressure is More than 12 bar

and operate alarm if both are High and green

Let if both are law.

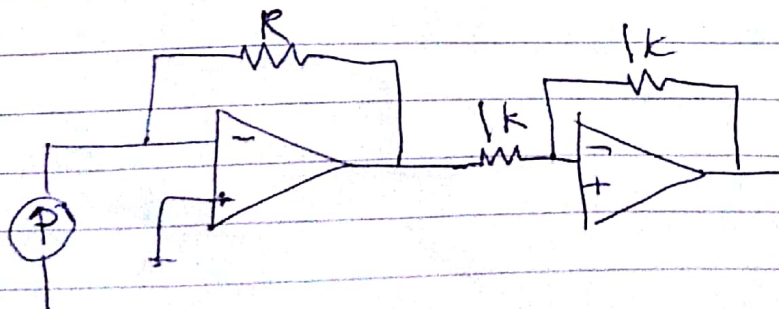

designed Point

Sensor maximum rang = $0.3 \text{ MA} \times 35 = 10.5 \text{ MA}$

Using $R = 500$

Sensor output = $10.5 \text{ mA} \times 500 = 5.25 \text{ V}$

Pressure output at designed point:-

$$4.2 \text{ mV} \times 12 = \boxed{50.4 \text{ mV}}$$

